

FREE

IEEE - CSULB Branch
March 19, 2021
Kiyo Terao
John Abraham


Agenda

- Project
- Kirchhoff's Laws
- Voltage Division
- Current Division
- OP Amp (Operational Amplifier)
- Switches
- Speakers

FREE

Project- Arduino Piano

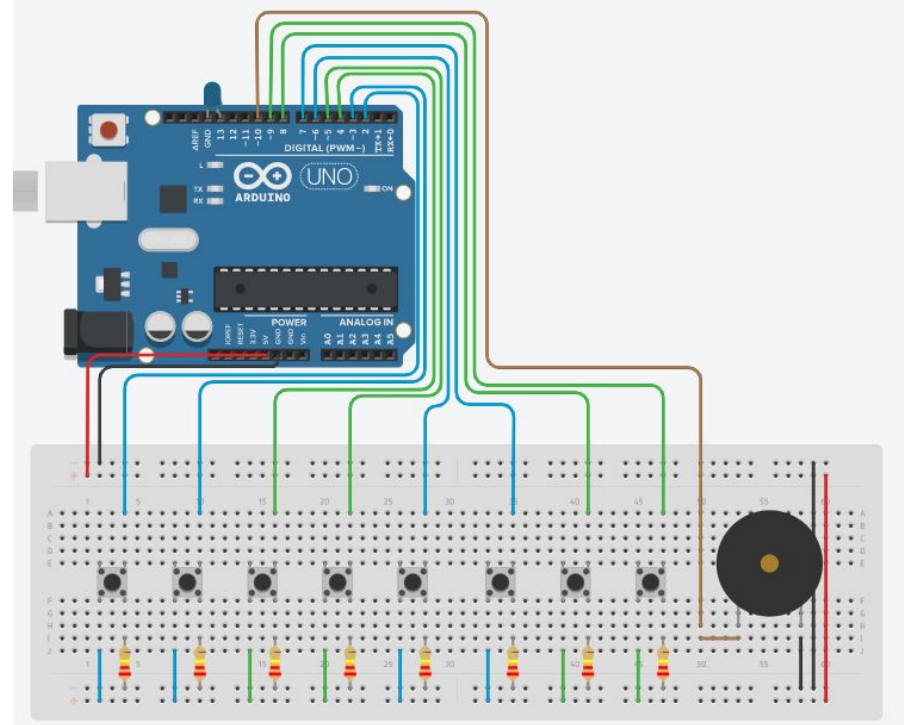- Sound Reactive Arduino Floor Piano
- Modules used
 - Arduino Uno/nano
- Components
 - Resistors
 - Jumper wires
 - Piezo




Voltage Division

- ▶ What is Voltage Division
 - A way to determine the voltage for a component within a circuit
 - Notice resistors are in series
 - V1 is the voltage for R1
 - V2 is the voltage for R2
 - Recall kirchoff's law of voltages, $-V_s + V_1 + V_2 = 0$
 - Or $V_1 + V_2 = V_s$

$$V_1 = \frac{R_1}{R_1 + R_2} V_s$$

$$V_2 = \frac{R_2}{R_1 + R_2} V_s$$

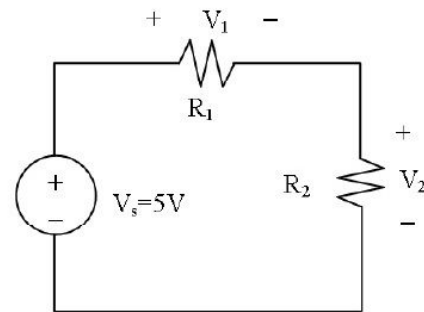


Current Division

- ▶ What is Current Division
 - A way to determine the voltage for a component within a circuit
 - Notice resistors are in parallel
 - I_1 is the current for R_1
 - I_2 is the current for R_2
 - Recall kirchoff's law of current at top node, $-I_s + I_1 + I_2 = 0$
 - Or $I_1 + I_2 = I_s$

Current Division Rule

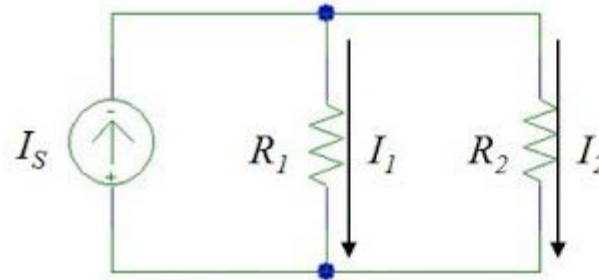- To calculate the current going through each resistor, use the following equations:



©ALL RIGHTS RESERVED.THE ELECTROBASIX.COM



$$I_1 = \frac{R_2}{R_1 + R_2} I_s$$
$$I_2 = \frac{R_1}{R_1 + R_2} I_s$$

Kirchhoff's Law - current

- ▶ What is Kirchhoff's Current Law
 - The net sum of current going through a node is equal to 0.
 - $i_1 + i_2 - i_3 - i_4 = 0$
 - Notice sign of corresponding current is related to direction of current arrow.
 - i_1 and i_2 are going towards node
 - i_3 and i_4 are going away from node
 - i_1 and i_2 are positive, i_3 and i_4 are negative


KIRCHHOFF'S LAWS

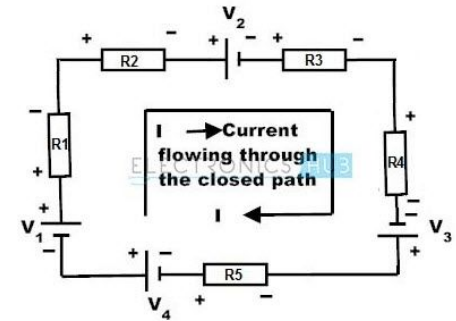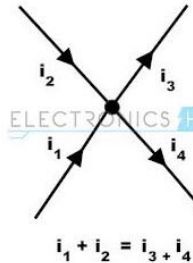Kirchhoff's Current Law (KCL) & Kirchhoff's Voltage Law (KVL)



Kirchhoff's Law of Current - Continued (Example)

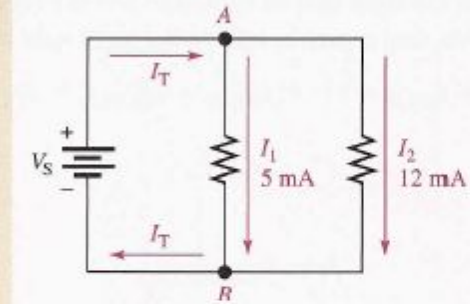- ▶ Apply Kirchhoff's law of Current at node A
 - $i_T - i_1 - i_2 = 0$
- ▶ Substitute the given values
 - $i_T - 5 - 12 = 0$
- ▶ Solve for i_T
 - $i_T = 17$



The total current out of node A is the sum of the two branch currents. So the total current into node A is

$$I_T = I_1 + I_2 = 5 \text{ mA} + 12 \text{ mA} = 17 \text{ mA}$$

The total current entering node B is the sum of the two branch currents. So the total current out of node B is

$$I_T = I_1 + I_2 = 5 \text{ mA} + 12 \text{ mA} = 17 \text{ mA}$$



Note that this equation can be equivalently expressed as $I_T - I_1 - I_2 = 0$.

Kirchhoff's Law - voltage

- ▶ What is Kirchhoff's Voltage Law
 - Voltage law
- The net sum of voltage going through closed loop is equal to 0.
- Ex:
 - $-v_1 + v_2 - v_3 + v_4 = 0$
 - Notice sign of corresponding voltage is first sign seen going in clockwise direction.
 - v_1 and v_3 are negative, v_2 and v_4 are positive

KIRCHHOFF'S LAWS

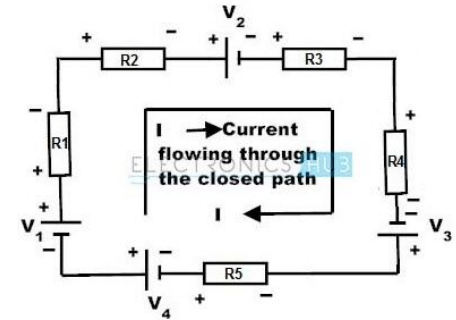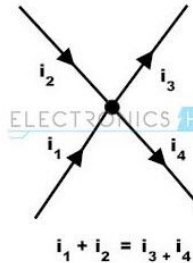Kirchhoff's Current Law (KCL) & Kirchhoff's Voltage Law (KVL)



Kirchhoff's Law of Voltage - Continued (Example)

- ▶ Formula


- $V_s + (-IR_1) + (-IR_2) = 0$
- $V_s = IR_1 + IR_2$

- ▶ Factor

- $V_s = I(R_1 + R_2)$


- ▶ Solve

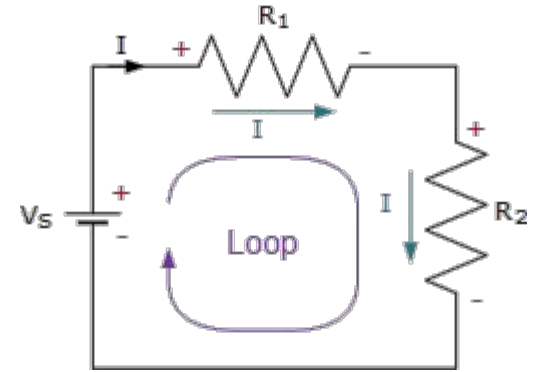- $V_s = IR_t$
- $R_t = R_1 + R_2$
- $I = V_s / R_t = V_s / R_1 + R_2$
- $V_{r1} = IR_1 = V_s (R_1 / R_1 + R_2)$
- $V_{r2} = IR_2 = V_s (R_2 / R_1 + R_2)$




Operational Amplifier (OP Amp)

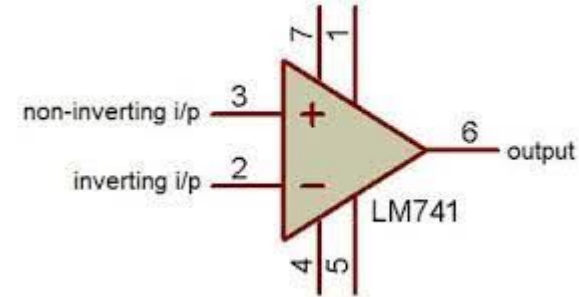- ▶ What is an OP Amp
 - A voltage amplifying device
- ▶ What an OP Amp can do ?
 - It can amplify weak electric signals
 - Used with external feedback components
 - Resistors
 - Capacitor



Operational Amplifier (OP Amp) - Continued

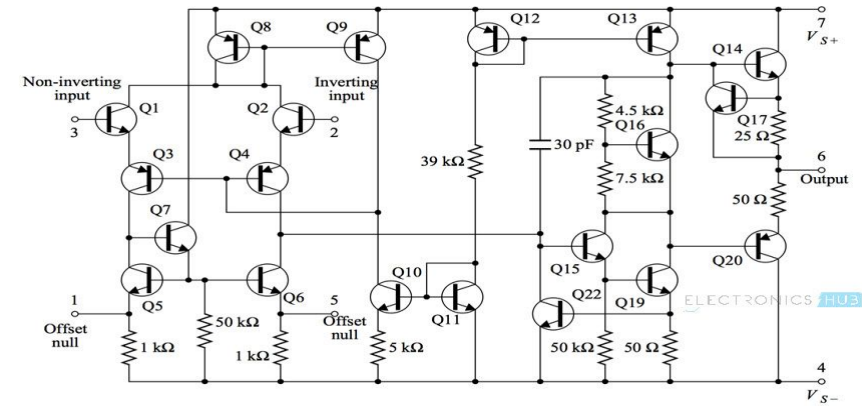
- ▶ LM741 IC Chip
 - 20 transistor
 - 11 resistor



Internal Circuitry of 741 Op-Amp IC

Operational Amplifier (OP Amp) - Continued

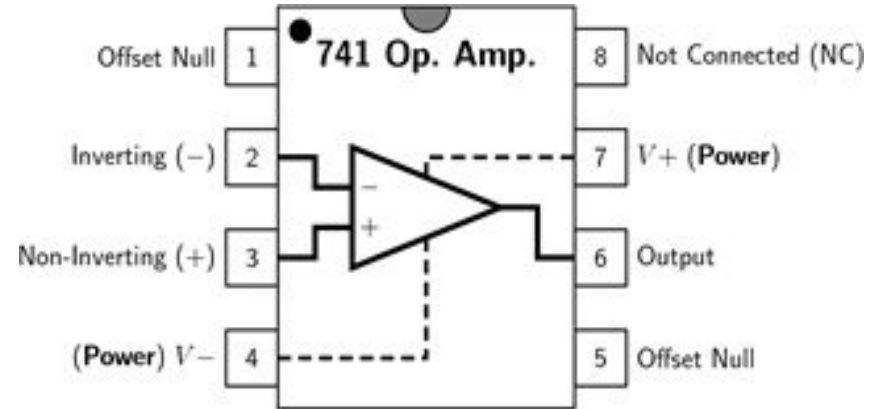- ▶ Pin Configuration
 - 8-Pin layout
 - Notice there are two inputs, inverting input(pin 2), and non-inverting input(pin 3)



Operational Amplifier (OP Amp) - Continued


► Formulas

- Inverting Amplifier Circuit Using 741 Op Amp


- $(AV) = -(R2 / R1)$

- Non-Inverting Amplifier Circuit Using 741 Op Amp

- $(AV) = 1 + (R2 / R1)$

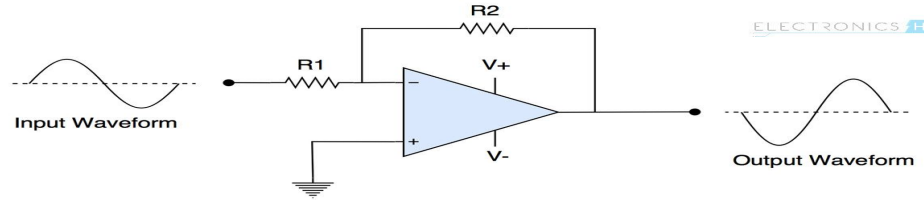


Inverting Voltage Amplifier using IC 741

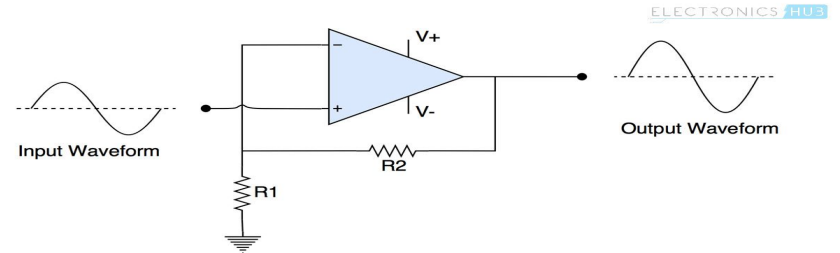

Non-Inverting Voltage Amplifier using IC 741


Switches (Push-Buttons)

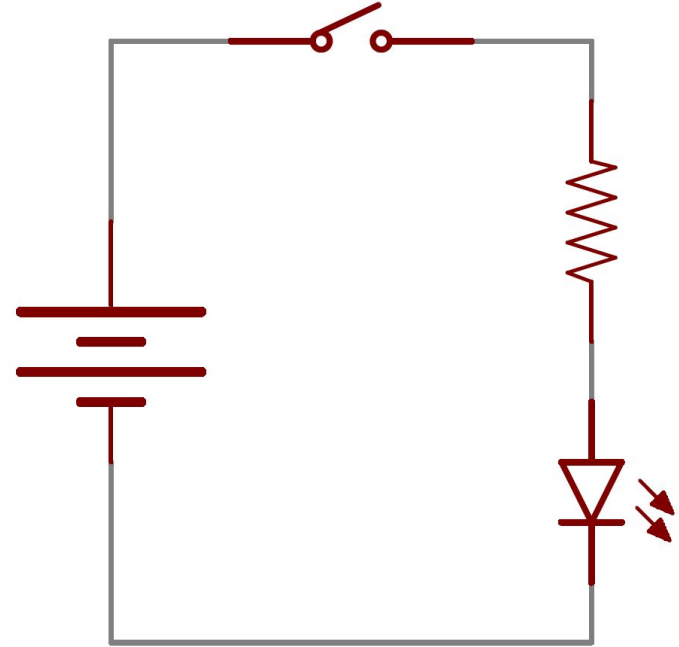- When a switch is closed, current is allowed to go through the pathway to allow the led diode to turn on
- When a switch is open, no current is able to go through the pathway, so the led diode is off.
- A switch is open or closed by pushing down on the button



Speakers

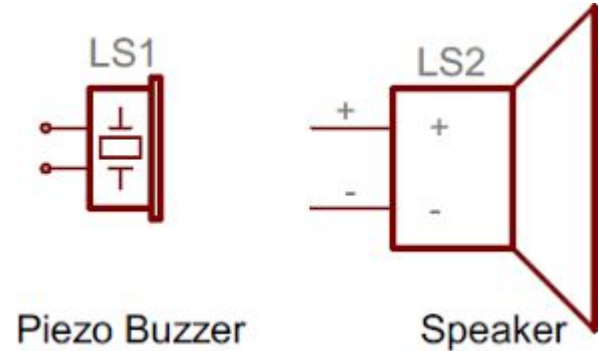
- ▶ What are speakers?
 - one of the most common output devices used by listeners
 - Produces audio output
 - convert electromagnetic waves into sound waves
 - Receive audio input
 - Digital
 - Analog



Speakers-continued

- ▶ How speakers work

-

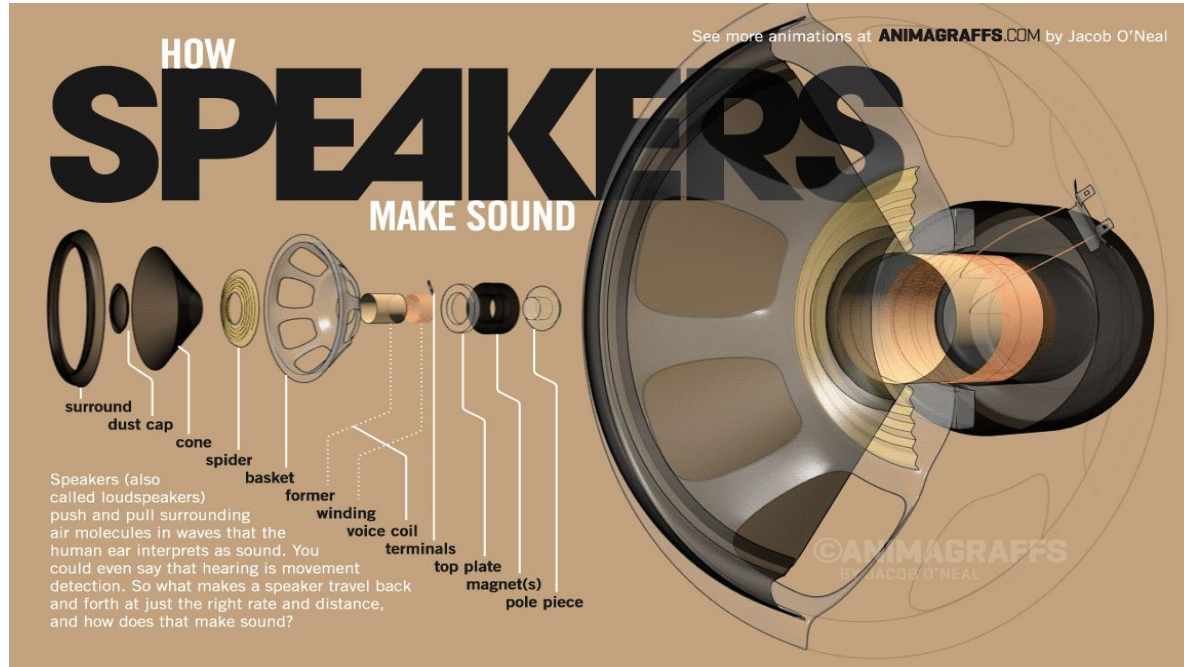

References

<https://www.electronics-tutorials.ws/dccircuits/voltage-divider.html>

<https://www.electronics-tutorials.ws/dccircuits/current-divider.html>

<https://byjus.com/physics/kirchhoffs-law/>

https://www.electronics-tutorials.ws/opamp/opamp_1.html

